



# Verilog HDL电路设计指导书

(仅供内部使用)

文档作者:	<u>verilog group</u>	日期:	<u>  /  /  </u>
项目经理:	<u>                    </u>	日期:	<u>  /  /  </u>
研 究 部:	<u>                    </u>	日期:	<u>  /  /  </u>
总 体 组:	<u>                    </u>	日期:	<u>  /  /  </u>
文档管理员:	<u>                    </u>	日期:	<u>  /  /  </u>



深圳市华为技术有限公司

版权所有 不得复制



修订记录

日期	修订版本	描述	作者
2000/04/04	1.00	初稿完成	Verilog_group



## 目 录

1典型电路的设计	4
1.1全加器的设计	4
1.2数据通路:	4
1.2.1四选一的多路选择器	4
1.2.2译码器	5
1.2.3优先编码器	6
1.3计数器	7
1.4算术操作	7
1.5逻辑操作	8
1.6移位操作	9
1.7时序器件	9
1.7.1上升沿触发的触发器	10
1.7.2带异步复位、上升沿触发的触发器	10
1.7.3带异步置位、上升沿触发的触发器	11
1.7.4带异步复位和置位、上升沿触发的触发器	11
1.7.5带同步复位、上升沿触发的触发器	12
1.7.6带同步置位、上升沿触发的触发器	12
1.7.7带异步复位和时钟使能、上升沿触发的触发器	13
1.8ALU	14
1.9有限状态机(FSM)的设计	15
1.9.1概述	16
1.9.2One-hot 编码	19
1.9.3Binary 编码	22
2常用电路设计	26
2.1CRC校验码产生器的设计	26
2.1.1概述	26
2.1.2CRC校验码产生器的分析与硬件实现	26
2.1.3并行CRC-16校验码产生器的Verilog HDL编码	27
2.1.4串行CRC-16校验码产生器的Verilog HDL编码	29
2.1随机数产生电路设计	31
2.1.1概述	31
2.1.1伪随机序列发生器的硬件实现	31
2.1.28位伪随机序列发生器的Verilog HDL编码	31
2.2双端口RAM仿真模型	33
2.3同步FIFO的设计	34
2.3.1功能描述	34
2.3.2设计代码	34
2.4异步FIFO设计	38
2.4.1概述	38
2.4.2设计代码	38



关键词:

摘 要:

缩略语清单:

参考资料清单				
名称	作者	编号	发布日期	查阅地点或渠道

## 1 典型电路的设计

在本章节中，主要讲述触发器、锁存器、多路选择器、解码器、编码器、饱和/非饱和计数器、FSM等常用基本电路的设计。如果你是初学者，我们建议你从典型电路学起，如果你已经非常熟悉电路设计，我们建议你从第2章看起。

### 1.1 全加器的设计

```

/*****
Filename      :    fulladd.v
Author        :    Verilog_guop
Description    :    Example of a one-bit full add.
Revision      :    2000/02/29
Company       :    Verilog_group
*****/

module FULLADDR(Cout, Sum, Ain, Bin, Cin);
input          Ain, Bin, Cin;
output         Sum, Cout;

wire           Sum;
wire           Cout;
assign         Sum = Ain ^ Bin ^ Cin;    利用assign和与门 或门 异或门完成
assign         Cout = (Ain & Bin) | (Bin & Cin) | (Ain & Cin);
endmodule

```

## 1.2 数据通路:

### 1.2.1 四选一的多路选择器

```

/*****

```



```
Filename      :      mux.v
Author        :      Verilog_guop
Description    :      Example of a mux4-1.
Revision       :      2000/02/29
Company       :      Verilog_group
```

```
\*****/
```

```
module MUX( C,D,E,F,S,Mux_out);
input      C,D,E,F ;      //input
input  [1:0]  S ;      //select control
output      Mux_out ;      //result

reg Mux_out ;

//mux
always@(C or D or E or F or S)
begin
    case (S)      利用case语句完成多路选择器，其中S是控制选择信号
        2'b00 : Mux_out = C ;
        2'b01 : Mux_out = D ;
        2'b10 : Mux_out = E ;
        default : Mux_out = F ;
    endcase
end
endmodule
```

### 1.2.2 译码器

```
\*****/
```

```
Filename      :      decode.v
Author        :      Verilog_guop
Description    :      Example of a 3-8 decoder.
Revision       :      2000/02/29
Company       :      Verilog_group
```

```
\*****/
```

```
module DECODE(Ain,En,Yout);
input      En ;      //enable
input  [2:0]  Ain ;      //input code
output  [7:0]  Yout ;
```

```
reg [7:0] Yout ;
```



```

always@(En or Ain)
    begin
        if(!En)
            Yout = 8'b0 ;
        else
            case (Ain)  利用case语句完成译码器，其中Ain是地址
                3'b000 : Yout = 8'b0000_0001 ;
                3'b001 : Yout = 8'b0000_0010 ;
                3'b010 : Yout = 8'b0000_0100 ;
                3'b011 : Yout = 8'b0000_1000 ;
                3'b100 : Yout = 8'b0001_0000 ;
                3'b101 : Yout = 8'b0010_0000 ;
                3'b110 : Yout = 8'b0100_0000 ;
                3'b111 : Yout = 8'b1000_0000 ;
                default : Yout = 8'b0000_0000 ;
            endcase
        end
    end
endmodule

```

### 1.2.3 优先编码器

```

/*****
Filename      :      Prio-encoder.v
Author        :      Verilog_guop
Description    :      Example of a Priority Encoder.
Revision      :      2000/02/29
Company       :      Verilog_group
*****/

module PRIO_ENCODER (Cin, Din, Ein, Fin, Sin, Pout);
input          Cin, Din, Ein, Fin;    //input signals
input [1:0]    Sin;                  //input select control

output         Pout;                  //output select result

reg            Pout;

//Pout assignment
always @(Sin or Cin or Din or Ein or Fin)
begin
    if (Sin == 2'b 00)  利用if else结构实现优先编码

```



```
        Pout  = Cin;
    else if (Sin == 2'b01)
        Pout  = Din;
    else if (Sin == 2'b10 )
        Pout  = Ein;
    else
        Pout  = Fin;
end

endmodule // module prio_encode
```

### 1.3 计数器

```
/******\

    Filename      :      count_en.v
    Author        :      Verilog_guop
    Description    :      Example of a counter with enable.
    Revision      :      2000/02/29
    Company       :      Verilog_group

\*****/

module COUNT_EN(En,Clock,Reset,Out);
parameter          Width  =8 ;
parameter          U_DLY =1;
input              Clock , Reset , En ;
output [Width-1:0]  Out ;

reg    [Width-1:0]  Out ;
always@(posedge Clock or negedge Reset)
    if (!Reset)
        Out  <= 8'b0 ;
    else if (En)                利用if else结构实现加1计数器
        Out  <= #U_DLY Out + 1 ;
endmodule
```

### 1.4 算术操作

```
/******\

    Filename      :      arithmetic.v
    Author        :      Verilog_guop
    Description    :      Example of a arithmetic include +, -, *, /.
    Revision      :      2000/02/29

\*****/
```



Company : Verilog\_group

\\*\*\*\*\*/

```
module ARITHMETIC (A , B, Q1, Q2 ,Q3, Q4 );
input  [3:0]  A, B ;           //input operator
output [4:0]  Q1 ;             //output sum, with carry bit
output [3:0]  Q2;              //output subtract result
output [3:0]  Q3 ;             //output quotient
output [7:0]  Q4 ;             //product
```

```
reg  [4:0]  Q1 ;
reg  [3:0]  Q2 , Q3 ;
reg  [7:0]  Q4 ;
```

//arithmetic operate

always@(A or B)

begin

```
    Q1 = A+B ;
    Q2 = A-B ;
    Q3 = A/2 ;
    Q4 = A*B ;
```

直接利用+ - \* /实现算数操作

end

endmodule

## 1.5 逻辑操作

/\*\*\*\*\*

```
Filename      : relational.v
Author        : Verilog_guop
Description    : Example of a relational operate
Revision      : 2000/02/29
Company       : Verilog_group
```

\\*\*\*\*\*/

```
module RELATIONAL(A, B,Q1,Q2,Q3,Q4) ;
input  [3:0]  A , B ;           //operator
output      Q1 , Q2 , Q3 , Q4 ; //result
```

```
reg      Q1 , Q2 , Q3 , Q4 ;
```

//compare





```

always@(A or B)
    begin
        Q1    = A > B ;
        Q2    = A < B ;
        Q3    = A >= B ;
        if (A <= B)
            Q4    = 1 ;
        else
            Q4    = 0 ;
        end
    endmodule

```

## 1.6 移位操作

```

/*****\

Filename      :    shifter.v
Author        :    Verilog_guop
Description    :    Example of a shifter
Revision      :    2000/02/29
Company       :    Verilog_group

\*****/

module SHIFT (Data ,Q1, Q2) ;
input  [3:0]  Data ;
output [3:0]  Q1,Q2 ;

parameter    B = 2 ;
reg  [3:0]   Q1, Q2 ;
always@(Data)
begin
    Q1    = Data << B ;
    Q2    = Data >> B ;
end
endmodule

```

利用<< 和>> 实现左移和右移

## 1.7 时序器件

一个时序器件（指触发器或锁存器）就是一个一位存储器。锁存器是电平敏感存储器件，触发器是沿触发存储器件。



触发器也被称为寄存器，在程序中体现为对上升沿或下降沿的探测，VERILOG中采用如下方法表示：

(posedge Clk) ----- 上升沿

(negedge Clk) -----下降沿

下面给出各种不同类型触发器的描述。

### 1.7.1 上升沿触发的触发器

```

/*****
Filename      :    dff.v
Author        :    Verilog_gruop
Description    :    Example of a Rising Edge Flip-Flop.
Revision      :    2000/03/30
Company       :    Verilog_group
*****/

module DFF (Data, Clk, Q);
input      Data, Clk;
output     Q;

reg        Q;
always @ (posedge Clk)
    Q  <= Data;
endmodule

```

### 1.7.2 带异步复位、上升沿触发的触发器

```

/*****
Filename      :    dff_async_rst.v
Author        :    Verilog_gruop
Description    :    Example of a Rising Edge Flip-Flop with Asynchronous Reset.
Revision      :    2000/03/30
Company       :    Verilog_group
*****/

module DFF_ASYNC_RST (Data, Clk, Reset, Q);
input      Data, Clk, Reset;
output     Q;
parameter  U_DLY =1;

```



```
reg Q;
always @(posedge Clk or negedge Reset)
    if (~Reset)
        Q    <= #U_DLY 1'b0 ;
    else
        Q    <= #U_DLY Data ;
endmodule
```

### 1.7.3 带异步置位、上升沿触发的触发器

```
/******\
Filename      :    dff_async_pre.v
Author       :    Verilog_gruop
Description   :    Example of a Rising Edge Flip-Flop with Asynchronous Preset.
Revision     :    2000/03/30
Company      :    Verilog_group
\*****/

module DFF_ASYNC_PRE (Data, Clk, Preset, Q);
input      Data, Clk, Preset;
output     Q;
parameter  U_DLY =1;
reg Q;
always @(posedge Clk or negedge Preset)
    if (~Preset)
        Q    <= #U_DLY 1'b1 ;
    else
        Q    <= #U_DLY Data ;
endmodule
```

利用if else结构实现带置位复位的触发器

### 1.7.4 带异步复位和置位、上升沿触发的触发器

```
/******\
Filename      :    dff_async.v
Author       :    Verilog_gruop
Description   :    Example of a Rising Edge Flip-Flop
                  with Asynchronous Reset and Preset.
Revision     :    2000/03/30
Company      :    Verilog_group
```



```
\*****/
```

```
module DFF_ASYNC (Data, Clk, Reset, Preset, Q);
input      Data, Clk, Reset, Preset ;
output     Q;
parameter  U_DLY = 1;
reg        Q;
always @(posedge Clk or negedge Reset or posedge Preset)
    if ( ~Reset)
        Q      <= 1'b0 ;
    else if (preset )
        Q      <= 1'b1;
    else
        Q      <= #U_DLY Data ;
endmodule
```

### 1.7.5 带同步复位、上升沿触发的触发器

```
/*****\
```

```
Filename      :    dff_sync_rst.v
Author        :    Verilog_gruop
Description    :    Example of a Rising Edge Flip-Flop with Synchronous Reset.
Revision      :    2000/03/30
Company       :    Verilog_group
```

```
\*****/
```

```
module DFF_SYNC_RST (Data, Clk, Reset, Q);
input      Data, Clk, Reset;
output     Q;
parameter  U_DLY = 1;
reg        Q;
always @(posedge Clk )
    if ( ~Reset)
        Q      <= #U_DLY 1'b0 ;
    else
        Q      <= #U_DLY Data ;
endmodule
```

异步和同步的区别，异步的话复位位置信号也在敏感列表中

### 1.7.6 带同步置位、上升沿触发的触发器



```
/******\
Filename      :      dff_sync_pre.v
Author        :      Verilog_guop
Description    :      Example of a Rising Edge Flip-Flop with Synchronous Preset.
Revision      :      2000/03/30
Company       :      Verilog_group
\*****/
```

```
module DFF_SYNC_PRE (Data, Clk, Preset, Q);
input      Data, Clk, Preset;
output     Q;
parameter  U_DLY = 1;
reg        Q;
always @ (posedge Clk )
    if ( ~Preset)
        Q      <= #U_DLY 1'b1 ;
    else
        Q      <= #U_DLY Data ;
endmodule
```

#### 1.7.7 带异步复位和时钟使能、上升沿触发的触发器

```
/******\
Filename      :      dff_ck_en.v
Author        :      Verilog_guop
Description    :      Example of a Rising Edge Flip-Flop with Asynchronous Reset
                    and Clock Enable.
Revision      :      2000/03/30
Company       :      Verilog_group
\*****/
```

```
module DFF_CK_EN (Data, Clk, Reset, En, Q);
input      Data, Clk, Reset, En;
output     Q;
parameter  U_DLY = 1;
reg        Q;
always @ (posedge Clk or negedge Reset)
    if ( ~Reset)
        Q      <= 1'b0 ;
    else if (En)
```



```
Q      <= #U_DLY Data ;
```

```
endmodule
```

## 1.8 ALU 算术逻辑单元 (Arithmetic Logic Unit, ALU)

```

\*****
Filename      :      alu.v
Author        :      Verilog_gruop
Description    :      Example of a 4-bit Carry Look Ahead ALU
Revision      :      2000/02/29
Company       :      Verilog_group
\*****

module ALU(A, B, Cin, Sum, Cout, Operate, Mode);
//input signals
input  [3:0]  A, B;          // two operands of ALU
input        Cin;           //carry in at the LSB      四位加法器
input  [3:0]  Operate;       //determine f(.) of sum = f(a, b)
input        Mode;          //arithmetic(mode = 1'b1) or logic operation(mode = 1'b0)
output [3:0]  Sum;           //result of ALU
output       Cout;          //carry produced by ALU operation

// carry generation bits and propogation bits.
wire  [3:0]  G, P;

// carry bits;
reg   [2:0]  C;

// function for carry generation:
function gen
input        A, B;
input  [1:0]  Oper;

begin
    case(Oper)
        2'b00: gen = A;
        2'b01: gen = A & B;
        2'b10: gen = A & (~B);
        2'b11: gen = 1'b0;
    endcase;
end
endfunction

// function for carry propergation:
function prop
input        A, B;
input  [1:0]  Oper;

```



```
begin
  case(Oper)
    2'b00: prop = 1;
    2'b01: prop = A | (~B);
    2'b10: prop = A | B;
    2'b11: prop = A;
  endcase;
end
endfunction

// producing carry generation bits;
assign G[0] = gen(A[0], B[0], Oper[1:0]);
assign G[1] = gen(A[1], B[1], Oper[1:0]);
assign G[2] = gen(A[2], B[2], Oper[1:0]);
assign G[3] = gen(A[3], B[3], Oper[1:0]);

// producing carry propogation bits;
assign P[0] = por(A[0], B[0], Oper[3:2]);
assign P[1] = por(A[1], B[1], Oper[3:2]);
assign P[2] = por(A[2], B[2], Oper[3:2]);
assign P[3] = por(A[3], B[3], Oper[3:2]);

// producing carry bits with carry-look-ahead;
always @(G or P or Cin, Mode)
begin
  if (Mode) begin
    C[0] = G[0] | P[0] & Cin;
    C[1] = G[1] | P[1] & G[0] | P[1] & P[0] & Cin;
    C[2] = G[2] | P[2] & G[1] | P[2] & P[1] & G[0] | P[2] & P[1] & P[0] & Cin;
    Cout = G[3] | P[3] & G[2] | P[3] & P[2] & G[1] | P[3] & P[2] & P[1] & G[0] | P[3] &
      P[2] & P[1] & P[0] & Cin;
  end
  else begin
    C[0] = 1'b0;
    C[1] = 1'b0;
    C[2] = 1'b0;
    Cout = 1'b0;
  end
end

// calculate the operation results;
assign Sum[0] = (~G[0] & P[0]) ^ Cin;
assign Sum[1] = (~G[1] & P[1]) ^ C[0];
assign Sum[2] = (~G[2] & P[2]) ^ C[1];
assign Sum[3] = (~G[3] & P[3]) ^ C[2];

endmodule
```

## 1.9 有限状态机 (FSM) 的设计

### 1.9.1 概述

有限状态机（FSM）是一种常见的电路，由时序电路和组合电路组成。**设计有限状态机的第一步是确定采用Moore状态机还是采用Mealy状态机。**（**Mealy型：**状态的转变不仅和当前状态有关，而且跟各输入信号有关；**Moore型：**状态的转变只和当前状态有关）。从实现电路功能来讲，任何一种都可以实现同样的功能。但他们的输出时序不同，所以，在选择使用那种状态机时要根据具体情况而定，在此，把他们的主要区别介绍一下：

**1. Moore状态机：**在时钟脉冲的有限个门延时之后，输出达到稳定。输出会在一个完整的时钟周期内保持稳定值，即使在该时钟内输入信号变化了，输出信号也不会变化。输入对输出的影响要到下一个时钟周期才能反映出来。把输入和输出分开，是Moore状态机的重要特征。

**2. Mealy状态机：**由于输出直接受输入影响，而输入可以在时钟周期的任一时刻变化，这就使得输出状态比Moore状态机的输出状态提前一个周期到达。输入信号的噪声可能会出现在输出信号上。

**3. 对同一电路，使用Moore状态机设计可能会比使用Mealy状态机多出一些状态。**

根据他们的特征和要设计的电路的具体情况，就可以确定使用那种状态机来实现功能。一旦确定状态机，接下来就要构造**状态转换图**。现在还没有一个成熟的系统化状态图构造算法，所以，对于实现同一功能，可以构造出不同的状态转换图。但一定要遵循结构化设计。在构造电路的状态转换图时，使用互补原则可以帮助我们检查设计过程中是否出现了错误。互补原则是指离开状态图节点的所有支路的条件必须是互补的。同一节点的任何2个或多个支路的条件不能同时为真。同时为真是我们设计不允许的。

在检查无冗余状态和错误条件后，就可以开始用verilog HDL来设计电路了。

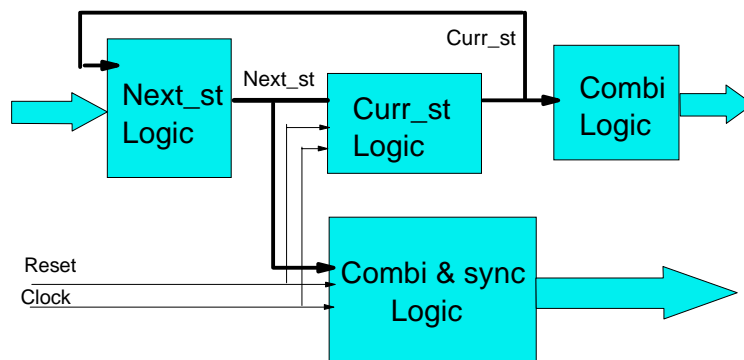


图1 状态机电路逻辑图

在设计的过程中要注意一下方面：

#### 1. full\_case spec

**定义完全状态，即使有的状态可能在电路中不会出现。**目的是避免综合出不希望的Latch，因为Latch可能会带来：a. 额外的延时；b. 异步Timing问题

```
always @(Curr_st)
begin
```



```

case(Curr_st)
  ST0 : Next_st = ST1;
  ST1 : Next_st = ST2;
  ST2 : Next_st = ST0;
endcase
end

```

 


图2 没有采用full-case

```

always @(Curr_st)
begin
  case(Curr_st) //synthesis full_case
    ST0 : Next_st = ST1;
    ST1 : Next_st = ST2;
    ST2 : Next_st = ST0;
    default : Next_st = ST0;
  endcase
end

```

 


图3 采用full-case 使用default项

## 2. parallel\_case spec

确保不同时出现多种状态

```
case({En3, En2, En1})
  3'b??1 : Out = In1;
  3'b?1? : Out = In2;
  3'b1?? : Out = In3;
endcase
```

 


图4 没采用parallel-case

```
case({En3, En2, En1}) //synthesis parallel_case
  3'b??1 : Out = In1;
  3'b?1? : Out = In2;
  3'b1?? : Out = In3;
endcase
```

 


图5 采用parallel-case

### 3. 禁止使用casex

casex在综合时，认为Z, X为Dont cares，会导致前仿真和后仿真不一致。如果电路中出现X，一定要分析是否会传递。

4. 推荐在模块划分时，把状态机设计分离出来，便于使用综合根据对状态机优化。

5. 在条件表达式或赋值语句中，要注意向量的宽度适配。否则，前仿真和后仿真不一致，RTL级的功能验证很难找出问题所在。

下图是一个状态机的状态转换图，在Verilog HDL中我们可以用如下方法设计该状态机。

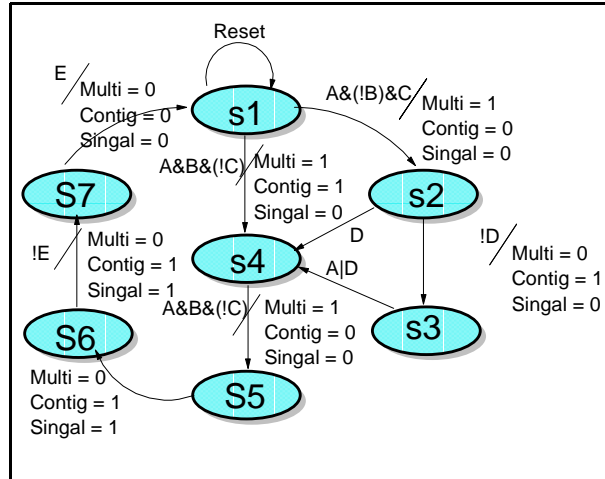


图4 状态转换图

## 1.9.2 One-hot 编码

```

/*****
Filename      :      one_hot_fsm.v
Author       :      Verilog_guop
Description   :      Example of a one-hot encoded state machine.
Revision     :      2000/02/29
Company      :      Verilog_group
*****/

module ONE_HOT_FSM (Clock, Reset, A, B, C, D, E,
                    Single, Multi, Contig);

input      Clock;                //system Clock
input      Reset;                //async Reset, active high
input      A, B, C, D, E;        //FSM input signals
output     Single, Multi, Contig; //FSM output signals

//define output signals type
reg        Single;
reg        Multi;
reg        Contig;

// Declare the symbolic names for states
parameter  [6:0]          // enum STATE_TYPE one-hot
            S1      = 7'b00000001,
            S2      = 7'b00000010,

```



```
S3      = 7'b0000100,
S4      = 7'b0001000,
S5      = 7'b0010000,
S6      = 7'b0100000,
S7      = 7'b1000000;

parameter U_DLY      = 1;

// Declare current state and next state variables
reg      [2:0]  Curr_st;
reg      [2:0]  Next_st;

//Curr_st assignment, sequential logic
always @ (posedge Clock or posedge Reset)
begin
    if (Reset)
        Curr_st      <= S1;
    else
        Curr_st      <= #U_DLY Next_st;
end

//combinational logic
always @ (Curr_st or A or B or C or D or D or E)
begin
    case (Curr_st)          //full_case
    S1 :
        begin
            Multi          = 1'b0;
            Contig          = 1'b0;
            Single          = 1'b0;
            if (A & ~B & C)
                Next_st      = S2;
            else if (A & B & ~C)
                Next_st      = S4;
            else
                Next_st      = S1;
        end
    S2 :
```



```
begin
Multi          = 1'b1;
Contig         = 1'b0;
Single         = 1'b0;
if (!D)
Next_st        = S3;
else
Next_st        = S4;
end

S3 :
begin
Multi          = 1'b0;
Contig         = 1'b1;
Single         = 1'b0;
if (A | D)
Next_st        = S4;
else
Next_st        = S3;
end

S4 :
begin
Multi          = 1'b1;
Contig         = 1'b1;
Single         = 1'b0;
if (A & B & ~C)
Next_st        = S5;
else
Next_st        = S4;
end

S5 :
begin
Multi          = 1'b1;
Contig         = 1'b0;
Single         = 1'b0;
Next_st        = S6;
end

S6 :
```



```
begin
    Multi      = 1'b0;
    Contig     = 1'b1;
    Single     = 1'b1;
    if (!E)
        Next_st = S7;
    else
        Next_st = S6;
    end
S7 :
    begin
        Multi      = 1'b0;
        Contig     = 1'b1;
        Single     = 1'b0;
        if (E)
            Next_st = S1;
        else
            Next_st = S7;
        end
    endcase
end
endmodule
```

### 1.9.3 Binary 编码

```
/******\
Filename      :    binary_fsm.v
Description   :    Example of a binary encoded state machine.
Revision      :    2000/02/29
Company       :    Huawei Ltd.
\*****/

`timescale 1ns / 10ps
module binary (Clock, Reset, A, B, C, D, E,
               Single, Multi, Contig);
input      Clock;           //system Clock
input      Reset;           //async Reset, active high
input      A, B, C, D, E;    //FSM input signals
output     Single, Multi, Contig; //FSM output signals
```



```
//define output signals type
reg          Single;
reg          Multi;
reg          Contig;

// Declare the symbolic names for states
parameter    [2:0]          //enum STATE_TYPE binary
              S1      = 3'b001,
              S2      = 3'b010,
              S3      = 3'b011,
              S4      = 3'b100,
              S5      = 3'b101,
              S6      = 3'b110,
              S7      = 3'b111;
parameter    U_DLY = 1;

// Declare current state and next state variables
reg    [2:0]  Curr_st;
reg    [2:0]  Next_st;

//Curr_st assignment, sequential logic  时序逻辑
always @ (posedge Clock or posedge Reset)
begin
    if (Reset)
        Curr_st    <= S1;
    else
        Curr_st    <= #U_DLY Next_st;
end

//combinational logic  组合逻辑，状态转移图
always @ (Curr_st or A or B or C or D or D or E)
begin
    case (Curr_st)          //full_case
    S1 :
        begin
            Multi          = 1'b0;
            Contig          = 1'b0;
```



```
Single          = 1'b0;
if (A & ~B & C)
  Next_st       = S2;
else if (A & B & ~C)
  Next_st       = S4;
else
  Next_st       = S1;
end

S2 :
begin
Multi          = 1'b1;
Contig         = 1'b0;
Single         = 1'b0;
if (!D)
  Next_st       = S3;
else
  Next_st       = S4;
end

S3 :
begin
Multi          = 1'b0;
Contig         = 1'b1;
Single         = 1'b0;
if (A | D)
  Next_st       = S4;
else
  Next_st       = S3;
end

S4 :
begin
Multi          = 1'b1;
Contig         = 1'b1;
Single         = 1'b0;
if (A & B & ~C)
  Next_st       = S5;
else
  Next_st       = S4;
```





```
        end
    S5 :
        begin
            Multi        = 1'b1;
            Contig        = 1'b0;
            Single        = 1'b0;
            Next_st       = S6;
        end
    S6 :
        begin
            Multi        = 1'b0;
            Contig        = 1'b1;
            Single        = 1'b1;
            if (!E)
                Next_st   = S7;
            else
                Next_st   = S6;
            end
        end
    S7 :
        begin
            Multi        = 1'b0;
            Contig        = 1'b1;
            Single        = 1'b0;
            if (E)
                Next_st   = S1;
            else
                Next_st   = S7;
            end
        end
    endcase
end
endmodule
```

以上介绍的用Verilog HDL设计来实现的FSM电路，可用下面的逻辑图来表现：

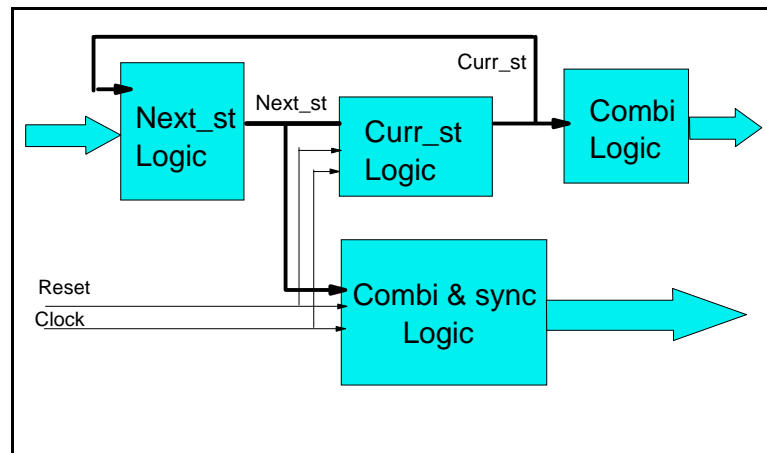


图5 FSM逻辑框图

## 2 常用电路设计

### 2.1 CRC校验码产生器的设计

#### 2.1.1 概述

冗余编码是在二进制通信系统中常用的差错检测方法，它是通过在原始数据后加冗余校验码来检测差错，冗余位越多，检测出传输错误的机率越大。循环冗余编码（Cyclic Redundancy Codes，简称CRC）是一种常用的冗余编码，CRC校验的基本原理是：CRC可由一称为生成多项式的常数去除该数据流的二进制数值而得，商数被放弃，余数作为冗余编码追加到数据流尾，产生新的数据流进行发送。在接收端，新的数据流被同一常数去除，检查余数是否为零。如果余数为零，就认为传输正确，否则就认为传输中已发生差错，该数据流重发。

#### 2.1.2 CRC校验码产生器的分析与硬件实现

在产生CRC校验码时，需要用到除法运算。一般说来，非常大的数字进行除法时，用数字逻辑实现时是比较麻烦的。因此，把二进制信息预先转换成一定的格式，这就是CRC的多项式表示。二进制数表示为生成多项式的系数，如下例所示：

$$1,0001,0000,0010,0001 = x^{16} + x^{12} + x^5 + 1$$

在多项式表示中，所有的二进制数均被表示成一个多项式，多项式的系数就是二进制中的对应值。D为数据流多项式，G为生成多项式，Q为商数多项式，R为余数多项式。在生成CRC校验码时，数据流多项式D被乘以 $X^n$ ，这里n为生成多项式G的最高次数，也就是CRC的长度。这个操作是通过将左移n位得到的，我们可以用CRC来代替多项式最后的n个0，组成新的数据流多项式。由于二进制的加法和减法是等价的，所以产生新的数据流多项式应能被生成多项式G除尽。用以下公式表示为：

$$(X^n \times D) + R = (Q \times G) + 0$$

在接收端，传输信息的前一部分为原始数据流D；后一部分（最后n位数）为余数R。整个数据流多项式被同一生成多项式G去除，商数被丢弃，余数应为0。如果余数不为0，说明传输数据时发生错误，数据需要重传。

不同的生成多项式有不同的检错能力，为了得到优化的结果，我们必须根据需求选择合适的生成多项式，CRC-16的生成多项式为：

$$G(x) = x^{16} + x^{12} + x^5 + 1$$

CRC校验码产生器分两种：串行CRC校验码产生器和并行CRC校验码产生器。本文用到的是并行CRC校验码产生器。由于计算并行CRC时用到了串行CRC的一些思想，所以在此先讲一下串行CRC的产生。

通常，CRC校验码的值可以通过线性移位寄存器和异或门求得，线性移位寄存器一次移一位，完成除法功能，异或门完成不带进位的减法功能。如果商数为'1'，则从被除数的高阶位减去除数，同时移位寄存器右移一位，准备为被除数的较低位进行运算。如果商数为'0'，则移位寄存器直接右移一位。串行CRC-16校验码产生器的原理图如图2所示。

 


图2 串行CRC-16校验码产生器原理图

在设计并行CRC校验码产生器的时候，我们可以采用串行CRC校验码的思想，用线性移位寄存器的方法产生并行CRC校验码。与串行CRC校验码产生器不同的是，并行CRC校验码产生器16位CRC同时输出，所以要求在一个时钟周期内，移位寄存器一次需要移16位。实际上，移位寄存器不可能在一个时钟周期内移16位，所以这部分电路是用组合逻辑来完成。整个CRC校验码产生器由组合逻辑和16个输出寄存器组成，通过仿真和综合，满足设计要求。

### 2.1.3 并行CRC-16校验码产生器的Verilog HDL编码

```

/*****
*      Filename : crc16_para.v
*      Author : Verilog group
*      Description : This module is used to check CRC_16 of 8-bits cell
*                   data, the generator polynomial is x^16+x^12+x^5+1.
*      Called by :
*      Revision History : 2000-5-5 Revision 1.0
*      Email : zhangnb@sz.huawei.com.cn
*      Company : Huawei Technology Inc.
*      Copyright(c) 1999,Huawei Technology Inc.,All right reserved.
*****/

```

```

//-----
// TOP MODULE

```



```
//-----
module CRC16_PARA(
    Reset , //Reset signal
    Gclk , //Clock signal
    Soc , //Start of cell
    Data_in , //input data of cell
    Crc_out //output CRC signal
);

//-----
// SIGNAL DECLARATIONS
//-----
input Reset ;
input Gclk ;
input Soc ;
input [7:0] Data_in ;
output [15:0] Crc_out ;

//-----
// SIGNAL DECLARATIONS
//-----
wire Reset ;
wire Gclk ;
wire Soc ;
wire [7:0] Data_in ;
reg [15:0] Crc_out ;

reg [15:0] Crc_tmp ;
reg Temp ;
integer i,j,k,l ;

//-----
// PARAMETERS
//-----
parameter U_DLY=1 ;

//-----
// Crc_out signal
//-----
always @(posedge Reset or posedge Gclk)
begin
    if (Reset)
        Crc_out <= #U_DLY 16'b0 ;
    else if (Soc == 1'b1)
        Crc_out <= #U_DLY 16'b0 ;
    else
        Crc_out <= #U_DLY Crc_tmp ;
end
```



```
//-----
// Crc_tmp signal
//-----
always @(Crc_out or Data_in)
begin
    Crc_tmp = Crc_out ;
    for (i=7;i>=0;i=i-1)
    begin
        Temp = Data_in[i] ^ Crc_tmp[15] ;

        for (j=15;j>12;j=j-1)
            Crc_tmp[j] = Crc_tmp[j-1] ;
        Crc_tmp[12] = Temp ^ Crc_tmp[11] ;

        for (k=11;k>5;k=k-1)
            Crc_tmp[k] = Crc_tmp[k-1] ;
        Crc_tmp[5] = Temp ^ Crc_tmp[4] ;

        for (l=4;l>0;l=l-1)
            Crc_tmp[l] = Crc_tmp[l-1] ;
        Crc_tmp[0] = Temp ;
    end
end

endmodule
```

#### 2.1.4 串行CRC-16校验码产生器的Verilog HDL编码

```
/*-----
*      Filename : crc16_ser.v
*      Author : Verilog group
*      Description : This module is used to check CRC_16 of serial data,
*                   the generator polynomial is  $x^{16}+x^{12}+x^5+1$ .
*      Called by :
*      Revision History : 2000-5-5 Revision 1.0
*      Email : zhangnb@sz.huawei.com.cn
*      Company : Huawei Technology Inc.
*      Copyright(c) 1999,Huawei Technology Inc.,All right reserved.
*-----*/

//-----
// TOP MODULE
//-----
module CRC16_SER(
    Reset , //Reset signal
    Gclk , //Clock signal
    Soc , //Start of cell
    Data_in , //input data of cell
    Crc_out //output CRC signal
);
```



```
//-----  
// SIGNAL DECLARATIONS  
//-----  
input      Reset  ;  
input      Gclk   ;  
input      Soc    ;  
input      Data_in ;  
output [15:0] Crc_out ;  
  
//-----  
// SIGNAL DECLARATIONS  
//-----  
wire      Reset  ;  
wire      Gclk   ;  
wire      Soc    ;  
wire      Data_in ;  
reg [15:0] Crc_out ;  
  
reg      Temp  ;  
integer  i,j,k,l ;  
  
//-----  
// PARAMETERS  
//-----  
parameter U_DLY=1  ;  
  
//-----  
// Crc_out signal  
//-----  
always @(posedge Reset or posedge Gclk)  
begin  
    if (Reset)  
        Crc_out <= #U_DLY 16'b0 ;  
    else if (Soc == 1'b1)  
        Crc_out <= #U_DLY 16'b0 ;  
    else  
        begin  
            Temp = Data_in ^ Crc_out[15] ;  
  
            for (j=15;j>12;j=j-1)  
                Crc_out[j] <= #U_DLY Crc_out[j-1] ;  
            Crc_out[12] <= #U_DLY Temp ^ Crc_out[11] ;  
  
            for (k=11;k>5;k=k-1)  
                Crc_out[k] <= #U_DLY Crc_out[k-1] ;  
            Crc_out[5] <= #U_DLY Temp ^ Crc_out[4]  ;  
  
            for (l=4;l>0;l=l-1)
```

```
Crc_out[l] <= #U_DLY Crc_out[l-1];
Crc_out[0] <= #U_DLY Temp      ;
end
end
```

```
endmodule
```

## 2.1 随机数产生电路设计

### 2.1.1 概述

伪随机序列又称为伪随机码，是一组人工生成的周期序列。它不仅具有随机序列的一些统计特性和高斯噪声所有的良好的自相关特征，而且具有某种确定的编码规则，同时又便于重复产生和处理，因而在通信领域应用广泛。

伪随机序列的产生方式很多，通常产生的伪随机序列的电路为一反馈移位寄存器。它又可分为线性反馈移位寄存器和非线性反馈移位寄存器两类。由线性反馈移位寄存器产生出的周期最长的二进制数字序列称为最大长度线性反馈移位寄存器序列，简称m序列，移位寄存器的长度为n，则m序列的周期为 $2^n-1$ ，没有全0状态。

其中，伪随机数发生器的初始状态由微处理器通过SEED寄存器给出。

#### 2.1.1 伪随机序列发生器的硬件实现

伪随机序列发生器的初始状态是由微处理器中SEED寄存器提供的，而SEED寄存器的位数为8位，所以需要设计一种8位的伪随机序列发生器，它的本原多项式为：

$$F(x) = x^8 + x^4 + x^3 + x^2 + 1$$

伪随机序列发生器结构如图1所示。

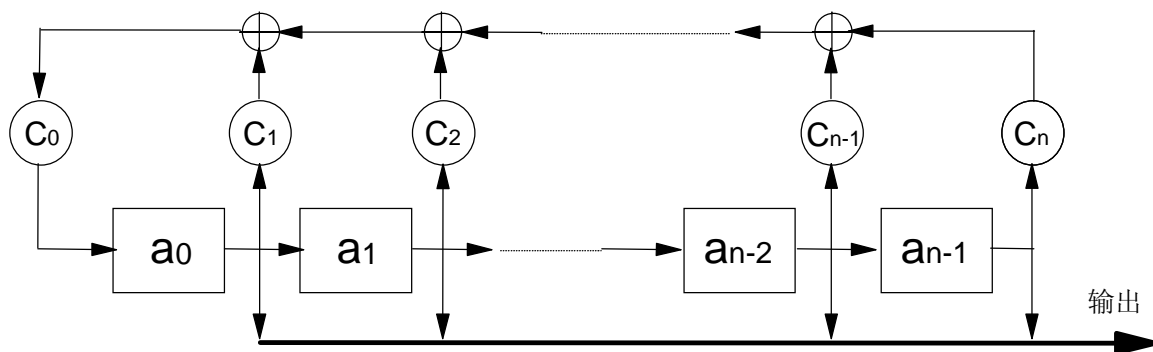


图2 伪随机序列发生器结构框图

图中Ci代表本原多项式F(x)中各项的系数。

#### 2.1.2 8位伪随机序列发生器的Verilog HDL编码

```
/*
*      Filename : rangen.v
*      Author : Verilog group
*/
```



```

*      Description : This module is used to generate 8-bits random number,
*                  the polynomial is  $x^8+x^4+x^3+x^2+1$ .
*      Called by :
*      Revision History : 2000-5-5
*                  Revision 1.0
*      Email : zhangnb@sz.huawei.com.cn
*      Company : Huawei Technology Inc.
*      Copyright(c) 1999,Huawei Technology Inc.,All right reserved.
*****/

```

```

//-----
// TOP MODULE
//-----
module RANGEN (
    Reset, //Reset signal
    Gclk , //Clock signal
    Load , //Load seed to Ran_num
    Seed , //initialize Ran_num
    Ran_num //output random number
);

```

```

//-----
// SIGNAL DECLARATIONS
//-----
input    Reset ;
input    Gclk  ;
input    Load  ;
input [7:0] Seed ;
output [7:0] Ran_num ;

```

```

//-----
// SIGNAL DECLARATIONS
//-----
wire     Reset ;
wire     Gclk  ;
wire     Load  ;
wire [7:0] Seed ;
reg [7:0] Ran_num ;
integer  i      ;

```

```

//-----
// PARAMETERS
//-----
parameter U_DLY=1 ;

```

```

//-----
// Ran_num signal
//-----

```





```

always @(posedge Reset or posedge Gclk)
begin
    if (Reset)
        Ran_num <= 8'b0 ;
    else if ( Load )
        Ran_num <= #U_DLY Seed;
    else
        begin
            for (i=1;i<8;i=i+1)
                Ran_num[i] <= #U_DLY Ran_num[i-1] ;
            Ran_num[0] <= #U_DLY Ran_num[1] ^ (Ran_num[2] ^ (Ran_num[3] ^
Ran_num[7]));
        end
    end
end

endmodule

```

## 2.2 双端口RAM仿真模型

用一个 512X8 的双端口 RAM 来实现同步 FIFO，该 RAM 的仿真模型如下所述：

```

/*****\

MODULE:      Dual Port RAM

FILE NAME:   dualram.v

VERSION:     2000-4-20

AUTHOR:

CODE TYPE:   Behavioral and RTL

DESCRIPTION: This module defines a Synchronous Dual Port
              Random Access Memory.

\*****/

module DUALRAM(
    Read_clock,
    Write_clock,
    Read_allow,
    Write_allow,
    Read_addr,
    Write_addr,
    Write_data,
    Read_data
);
parameter    DLY          1;    // Clock-to-output delay. Zero
                                   // time delays can be confusing
                                   // and sometimes cause problems.

```



```
parameter    RAM_WIDTH  8;      // Width of RAM (number of bits)
parameter    RAM_DEPTH  512;    // Depth of RAM (number of bytes)
parameter    ADDR_WIDTH 9;      // Number of bits required to
                                // represent the RAM address
```

```
input          Read_clock;      // RAM read clock
input          Write_clock;     // RAM write clock
input  [RAM_WIDTH-1:0] Write_data; // RAM data input
input  [ADDR_WIDTH-1:0] Read_addr; // RAM read address
input  [ADDR_WIDTH-1:0] Write_addr; // RAM write address
input          Read_allow;      // Read control
input          Write_allow;     // Write control
output [RAM_WIDTH-1:0] Read_data; // RAM data Output
reg  [RAM_WIDTH-1:0] Read_data;
```

```
reg  [RAM_WIDTH-1:0] Mem [RAM_DEPTH-1:0];
```

```
// Look at the rising edge of the clock
always @(posedge Write_clock) begin
    if (Write_allow)
        Mem[Write_addr] <= #DLY Write_data;
end
always @(posedge Read_clock) begin
    if (Read_allow)
        Read_data <= #DLY Mem[Read_addr];
end
endmodule
```

## 2.3 同步FIFO的设计

### 2.3.1 功能描述

下面的同步FIFO是上述的双端口RAM来实现的。由于读写是用同一个时钟，可以直接用FIFO长度计数器产生Empty和Full标志。执行一次写操作，长度计数器（Facntr）加1，执行一次写操作，Facntr减1。当下一次读地址等于写地址，并且只执行读操作时，将产生Empty标志；当下一次写地址等于读地址，并且只执行写操作时，将产生Full标志。

### 2.3.2 设计代码



/\*\*\*\*\*\*\

Filename : syncfifo.v  
Description : FIFO controller top level  
Implements a 512x8 FIFO with common read/write clocks.  
Author : Verilog Group  
Revision : 2000-04-20  
Company : Huawei Ltd.

\\*\*\*\*\*/

`timescale 1ns / 10ps

module SYNCFIFO(

Fifo\_rst, //async reset  
Clock, //write and read clock  
Read\_enable,  
Write\_enable,  
Write\_data,  
Read\_data,  
Full, //full flag  
Empty, //empty flag  
Fcounter //count the number of data in FIFO  
);

parameter DATA\_WIDTH = 8;

parameter ADDR\_WIDTH = 9;

input Fifo\_rst;  
input Clock;  
input Read\_enable;  
input Write\_enable;  
input [DATA\_WIDTH-1:0] Write\_data;  
output [DATA\_WIDTH-1:0] Read\_data;  
output Full;  
output Empty;  
output [ADDR\_WIDTH-1:0] Fcounter;

reg [DATA\_WIDTH-1:0] Read\_data;

reg Full;

reg Empty;



```

reg      [ADDR_WIDTH-1:0]  Fcounter;

reg      [ADDR_WIDTH-1:0]  Read_addr;    //read address
reg      [ADDR_WIDTH-1:0]  Write_addr;   //write address

wire     Read_allow = (Read_enable && !Empty);
wire     Write_allow = (Write_enable && ! Full);

/*****\

    BLOCK RAM instantiation for FIFO. Module is 512x8, of which one
    address location is sacrificed for the overall speed of the design

\*****/

DUALRAM U_RAM(
    Read_clock(Clock),
    Write_clock(Clock),
    Read_allow(Read_allow),
    Write_allow(Write_allow),
    Read_addr(Read_addr),
    Write_addr(Write_addr),
    Write_data(Write_data),
    Read_data(Read_data)
);

/*****\

    Empty flag is set on Fifo_rst (initial), or when on the
    next clock cycle, Write Enable is low, and either the
    FIFOcount is equal to 0, or it is equal to 1 and Read
    Enable is high (about to go Empty).

\*****/

always @(posedge Clock or posedge Fifo_rst)
    if (Fifo_rst)
        Empty <= 'b1;
    else
        Empty <= (! Write_enable && (Fcounter[8:1] == 8'h0) &&
            ((Fcounter[0] == 0) || Read_enable));

/*****\

    Full flag is set on Fifo_rst (but it is cleared on the
    first valid clock edge after Fifo_rst is removed), or
    when on the next clock cycle, Read Enable is low, and

```



```
either the FIFOcount is equal to 1FF (hex), or it is
equal to 1FE and the Write Enable is high (about to go Full).
\*****/
always @(posedge clock or posedge Fifo_rst)
    if (Fifo_rst)
        Full <= 'b1;
    else
        Full <= (! Read_enable && (Fcounter[8:1] == 8'hFF) &&
            ((Fcounter[0] == 1) || Write_enable));
/*****\

    Generation of Read and Write address pointers.
\*****/
always @(posedge clock or posedge Fifo_rst)
    if (Fifo_rst)
        Read_addr <= 'h0;
    else if (Read_allow)
        Read_addr <= Read_addr + 'b1;
always @(posedge clock or posedge Fifo_rst)
    if (Fifo_rst)
        Write_addr <= 'h0;
    else if (Write_allow)
        Write_addr <= Write_addr + 'b1;
/*****\

    Generation of FIFOcount outputs. Used to determine how
    Full FIFO is, based on a counter that keeps track of how
    many words are in the FIFO. Also used to generate Full
    and Empty flags. Only the upper four bits of the counter
    are sent outside the module
\*****/
always @(posedge clock or posedge Fifo_rst)
    if (Fifo_rst)
        Fcounter <= 'h0;
    else if ((! Read_allow && Write_allow) || (Read_allow && ! Write_allow))
        begin
            if (Write_allow) Fcounter <= Fcounter + 'b1;
            else Fcounter <= Fcounter - 'b1;
        end
end
```



endmodule

## 2.4 异步FIFO设计

### 2.4.1 概述

异步FIFO使用完全独立的读写时钟，Empty由读时钟产生，Full由写时钟产生，两者关系完全异步，所以不能采用同步FIFO中的计数器来产生Empty和Full信号。为解决这一问题，采用了将二进制地址转换为格雷码（Gray-code）地址的方法。

### 2.4.2 设计代码

```
/******\

Filename      :      asyncfifo.v
Description    :      Async FIFO controller top level
                  Implements a 512x8 FIFO with common read/write clocks.

Author        :      Verilog Group
Revision      :      2000-04-20
Company       :      Huawei Ltd.

\*****/

`timescale 1ns / 10ps
module ASYNCFIFO(
    Fifo_rst,          //async reset
    Read_clock,
    Write_clock,
    Read_enable,
    Write_enable,
    Write_data,
    Read_data,
    Full,              //Full flag
    Empty              //Empty flag
);

parameter          DATA_WIDTH = 8;
parameter          ADDR_WIDTH = 9;
input               Fifo_rst;
input               Read_clock;
input               Write_clock;
input               Read_enable;
input               Write_enable;
input               Write_data;
input [DATA_WIDTH-1:0] Read_data;

parameter          DATA_WIDTH = 8;
parameter          ADDR_WIDTH = 9;
input               Fifo_rst;
input               Read_clock;
input               Write_clock;
input               Read_enable;
input               Write_enable;
input               Write_data;
input [DATA_WIDTH-1:0] Read_data;
```



```

output [DATA_WIDTH-1:0]  Read_data;
output                   Full;
output                   Empty;
reg                      Full;
reg                      Empty;

reg [ADDR_WIDTH-1:0]     Write_addrgray;
reg [ADDR_WIDTH-1:0]     Write_nextgray;
reg [ADDR_WIDTH-1:0]     Read_addrgray;
reg [ADDR_WIDTH-1:0]     Read_nextgray;
reg [ADDR_WIDTH-1:0]     Read_lastgray;

wire                     Read_allow;
wire                     Write_allow;

/*****\

    BLOCK RAM instantiation for FIFO. Module is 512x8, of which one
    address location is sacrificed for the overall speed of the design.

\*****/

DUALRAM U_RAM(
    Read_clock(Read_clock),
    Write_clock(Write_clock),
    Read_allow(Read_allow),
    Write_allow(Write_allow),
    Read_addr(Read_addr),
    Write_addr(Write_addr),
    Write_data(Write_data),
    Read_data(Read_data)
);

/*****\

    Empty flag is set on Fifo_rst (initial), or when gray
    code counters are equal, or when there is one word in
    the FIFO, and a Read operation is about to be performed

\*****/

always @(posedge Read_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Empty <= 1'b1;
    else

```



```

Empty <= (Emptyg || (Almostemptyg && Read_enable && ! Empty));

/*****\

Full flag is set on Fifo_rst (initial, but it is cleared
on the first valid Write_clock edge after Fifo_rst is
de-asserted), or when Gray-code counters are one away
from being equal (the Write Gray-code address is equal
to the Last Read Gray-code address), or when the Next
Write Gray-code address is equal to the Last Read Gray-code
address, and a Write operation is about to be performed.

\*****/

always @(posedge Write_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Full <= 1'b1;
    else
        Full <= (Fullg || (Almostfullg && Write_enable && ! Full));

/*****\

Generation of Read address pointers. The primary one is
binary (read_addr), and the Gray-code derivatives are
generated via pipelining the binary-to-Gray-code result.
The initial values are important, so they're in sequence.
Grey-code addresses are used so that the registered
Full and Empty flags are always clean, and never in an
unknown state due to the asynchronous relationship of the
Read and Write clocks. In the worst case scenario, Full
and Empty would simply stay active one cycle longer, but
it would not generate an error or give false values.

\*****/

always @(posedge Read_clock or posedge Fifo_rst)
    if (Fifo_rst)
        read_addr <= 'b0;
    else if (read_allow)
        read_addr <= read_addr + 1;
always @(posedge Read_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Read_nextgray <= 9'b100000000;
    else if (read_allow)
        Read_nextgray <= { read_addr[8], (read_addr[8] ^ read_addr[7]),

```





```

        (read_addr[7] ^ read_addr[6]), (read_addr[6] ^ read_addr[5]),
        (read_addr[5] ^ read_addr[4]), (read_addr[4] ^ read_addr[3]),
        (read_addr[3] ^ read_addr[2]), (read_addr[2] ^ read_addr[1]),
        (read_addr[1] ^ read_addr[0]) };

always @(posedge Read_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Read_addrgray <= 9'b100000001;
    else if (read_allow)
        Read_addrgray <= Read_nextgray;
always @(posedge Read_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Read_lastgray <= 9'b100000011;
    else if (read_allow)
        Read_lastgray <= Read_addrgray;

/*****
    Generation of Write address pointers. Identical copy of *
    read pointer generation above, except for names. *
*****/

always @(posedge Write_clock or posedge Fifo_rst)
    if (Fifo_rst)
        write_addr <= 'b0;
    else if (write_allow)
        write_addr <= write_addr + 1;
always @(posedge Write_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Write_nextgray <= 9'b100000000;
    else if (write_allow)
        Write_nextgray <= { write_addr[8], (write_addr[8] ^ write_addr[7]),
        (write_addr[7] ^ write_addr[6]), (write_addr[6] ^ write_addr[5]),
        (write_addr[5] ^ write_addr[4]), (write_addr[4] ^ write_addr[3]),
        (write_addr[3] ^ write_addr[2]), (write_addr[2] ^ write_addr[1]),
        (write_addr[1] ^ write_addr[0]) };
always @(posedge Write_clock or posedge Fifo_rst)
    if (Fifo_rst)
        Write_addrgray <= 9'b100000001;
    else if (write_allow)
        Write_addrgray <= Write_nextgray;

```



```

\*****\

```

Allow flags determine whether FIFO control logic can \*  
operate. If Read\_enable is driven high, and the FIFO is \*  
not Empty, then Reads are allowed. Similarly, if the \*  
Write\_enable signal is high, and the FIFO is not Full, \*  
then Writes are allowed. \*

```

\*****/

```

```

assign read_allow = (Read_enable && ! Empty);

```

```

assign write_allow = (Write_enable && ! Full);

```

```

\*****\

```

When the Write/Read Gray-code addresses are equal, the  
FIFO is Empty, and Emptyg (combinatorial) is asserted.  
When the Write Gray-code address is equal to the Next  
Read Gray-code address (1 word in the FIFO), then the  
FIFO potentially could be going Empty (if Read\_enable is  
asserted, which is used in the logic that generates the  
registered version of Empty).

Similarly, when the Write Gray-code address is equal to  
the Last Read Gray-code address, the FIFO is Full. To  
have utilized the Full address space (512 addresses)  
would have required extra logic to determine Full/Empty  
on equal addresses, and this would have slowed down the  
overall performance. Lastly, when the Next Write Gray-  
code address is equal to the Last Read Gray-code address  
the FIFO is Almost Full, with only one word left, and  
it is conditional on Write\_enable being asserted.

```

\*****/

```

```

always @(Write_addrgray or Read_addrgray)

```

```

    if( Write_addrgray == Read_addrgray )

```

```

        Emptyg = 'b1;

```

```

    else

```

```

        Emptyg = 'b0;

```

```

always @(Write_addrgray or Read_nextgray)

```

```

    if( Write_addrgray == Read_nextgray )

```

```

        Almostemptyg = 'b1;

```

```

    else

```



```
        Almostemptyg = 'b0;  
always @(Write_addrgray or Read_lastgray)  
    if( Write_addrgray == Read_lastgray )  
        Fullg = 'b1;  
    else  
        Fullg = 'b0;  
always @(Write_nextgray or Read_lastgray)  
    if( Write_nextgray == Read_lastgray )  
        Almostfullg = 'b1;  
    else  
        Almostfullg = 'b0;  
endmodule
```



华为技术有限公司

请输入文档名称

机密  
请输入文档编号